


# ***ECE 467: Introduction VLSI Design***

## ***Project: Multiplication and Accumulation (MAC) Datapath for Neural Networks***

**Amit Ranjan Trivedi**

School of Electrical and Computer Engineering  
University of Illinois at Chicago

# System Goal

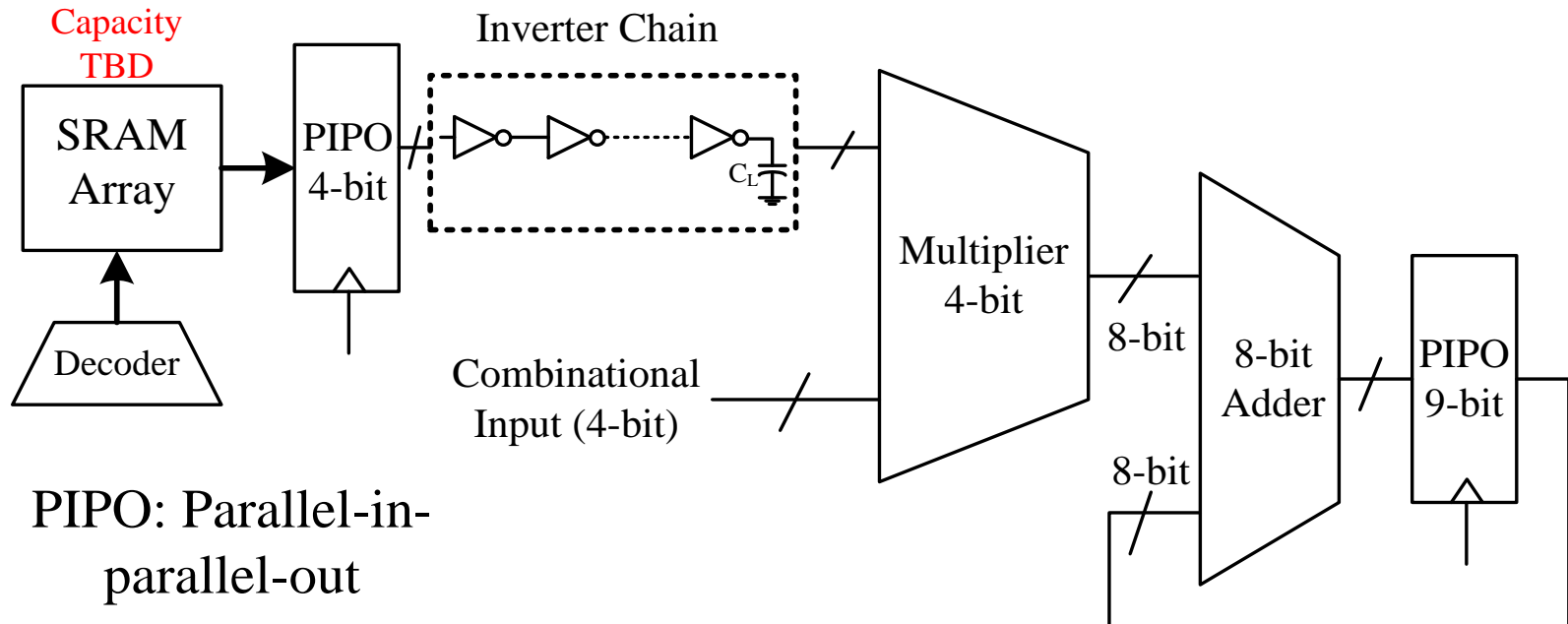

# *System Level Components*

- High level components
    - Inverter chain and universal gates
    - Adder
    - Multiplier
    - Register
    - SRAM
- TBD based on  
sequence in which  
topics are covered in  
lecture

# *Specifications*

- Technology: 45nm
- Nominal supply voltage: 0.9V-1.2V (choose appropriately to optimize the performance)
  - Targeted clock frequency: 1 GHz
- Aim-
  - Achieve functionality
  - Supply Voltage should be same for all the system blocks
  - Apply techniques learnt in the course to maximize frequency
  - **Low power design:** apply different power saving techniques to make your design energy efficient

# *Transistor Specifications*

- VTG: Regular threshold voltage transistor should be used for project design

# *Submission Schedule*

- Project Report I [5% of the total]: October 27<sup>th</sup>
- Project Report II [5% of the total]: November 17<sup>th</sup>
- Final Report [15% of the total]: December 9<sup>th</sup>
- Classroom Presentation [5% of the total]: Last week of classes

All report are due by the midnight of the due date

# *Tentative Project Plan*

- Part-1 (Schematic Design)
  - Inverter chain design and NAND, NOR, XOR implementation (including symbols)
  - Adder
  - Flip/Flop design
  - Multiplier design
  - SRAM design
- Part-2
  - System level integration

# *Tentative Submission Dates*

- Reports are due biweekly. Final grades for lab will be cumulative of these reports.
- Classroom presentations near the end of semester [TBD]
- This document will be updated biweekly. Please check this document regularly.




# *Project Report 1*

- *Design of Inverter Chain to drive larger loads:*
  - Memory blocks are often located far from the processing elements. Therefore, long interconnects are required for data transmission.
  - Using long interconnects leads to significant capacitive load at PIPO's output.
  - To drive larger loads efficiently, we use inverter chains

# *Project Report 1(contd..)*

- In this sub-project, we will be designing an inverter chain to efficiently drive larger loads.
- *Project Description:*
  - Let the input capacitance of a minimum sized inverter be  $C_1=10\text{fF}$
  - Determine the number of appropriately sized inverter stages required to drive a load of  $128C_1=1.28\text{pF}$ 
    - Refer to the lecture notes on sizing of inverter chain

# *Project Description(contd..)*

 

Number of stages (N)	Upsizing Factor ( $u$ )	Propagation delay ( $t_p$ )
1		
2		
3		
4		
5		

# *Project Report 1*

- Results required:
  - Delay characteristics for different N (Cadence plots) and complete the given table
  - Delay vs. Number of stages (N)
  - Delay vs. Supply Voltage (for optimal N)
  - Delay vs. Temperature (for optimal N)
  - Leakage current vs. Supply Voltage & Temperature (for optimal N)
  - Optimize the body biasing of all the NMOS transistors to minimize delay and plot Delay vs.  $V_{BS}$  ( $V_{BS}$  ranging - 0.25 to 0.25) (for optimal N) [All the NMOS will have same  $V_{BS}$ ]

# *Additional Assignment*

- Create a library of standard cells including 2-input NAND & NOR, 3-input NAND & NOR and 2-input EXOR [size these gates to match  $t_{\text{phl}}$  and  $t_{\text{plh}}$  characteristics with that of a minimum sized inverter. For all designs,  $L_p=L_n=L_{\text{min}}=45\text{nm}$ . Minimum sized inverter:  $W_{\text{min}}=2XL_{\text{min}}$ ,  $W_n=W_{\text{min}}$ ,  $W_p=2X W_{\text{min}}$ ]
- Create two more variants of the above setup as follows:
  - To match characteristics of an inverter upsized by a factor 2
  - To match characteristics of an inverter upsized by a factor 3

## *Some tips*

- Label everything appropriately (nodes, wires, instances), no default labels
- Minimum size inverter can be named as INVx1, and twice strength one as INVx2. Use similar naming convention for the other gates too.
- Write one-line description of the circuit in the schematic view
- Schematic should be easy to follow

# *Additional Assignment (contd..)*

- Results Required:
  - Delay vs. Supply Voltage
  - Delay vs. Temperature
  - Leakage current vs. Supply Voltage & Temperature
  - Optimize the body biasing of all the NMOS transistors to minimize delay and plot Delay vs.  $V_{BS}$  ( $V_B$  ranging -0.25 to 0.25)[All the NMOS will have same  $V_B$ ]

# *Project Report 2*

- Design 1-bit Full adder using
  - Architecture of your choice (design your schematic using expression in slides 6 & 7 of Adders lecture)
  - Static CMOS Full Adder architecture (Refer to slide 7)
  - Transmission Gate Based Full Adder architecture (Refer slide 11 & 12)



# *Project Report 2*

- Results required for adder design
  - Compare the area and delay performance of different Full Adder architectures and select the best architecture to work with
  - Delay vs. Supply Voltage
  - Delay vs. Temperature
  - Leakage current vs. Supply Voltage and Temperature

## *Project Report 2 (contd.)*

- Using the chosen Full Adder implementation style
  - Design an 8-bit Ripple Carry Adder (Refer Slide 15)
  - Design an 8-bit Carry Select Adder (Refer Slide 37)
  - Optimize one of the above designs to achieve a worst-case delay of  $< 500\text{ps}$  (i.e, design to retain functionality when  $C_{in}$  is switched at a frequency  $> 1.5\text{GHz}$ )

# *Project Report 2*

- Results required
  - Obtain proper functionality
  - Compare the area and delay performance of the two architectures
  - Determine and state the input combination for worst-case delay
  - Worst-Case Delay vs. Supply Voltage
  - Worst-Case Delay vs. Temperature
  - Leakage current vs. Supply Voltage and Temperature

# *Final Report*


- Design an SRAM cell
  - Design an 6T SRAM cell
  - Read Noise Margin  $\geq 30\%$  of VDD
  - Write Noise Margin  $\geq 30\%$  of VDD
  - Required results
    - Clearly show the design steps
    - Power Consumption vs. VDD and Temperature
    - Read and Write Noise Margin vs. VDD
    - Read and Write Noise Margin vs. Temperature

# *Final Report*

- Implement an array of 32x32 SRAM cells using 6T SRAM cells
- Design write circuitry and demonstrate data write ability of your design
- Design a row and column decoder to read 4-bit data while operating at clock frequency of >1GHz.
- **Note: For read operation, initialize array contents randomly or to a fixed value.**
- Consider bitline wire capacitance and word line wire capacitance to be 40fF (Does not scale with number of SRAM cells)
- Delay of the row and column decoder should be  $< T_{CLK}/2$

# Final Report

- SRAM timing considerations

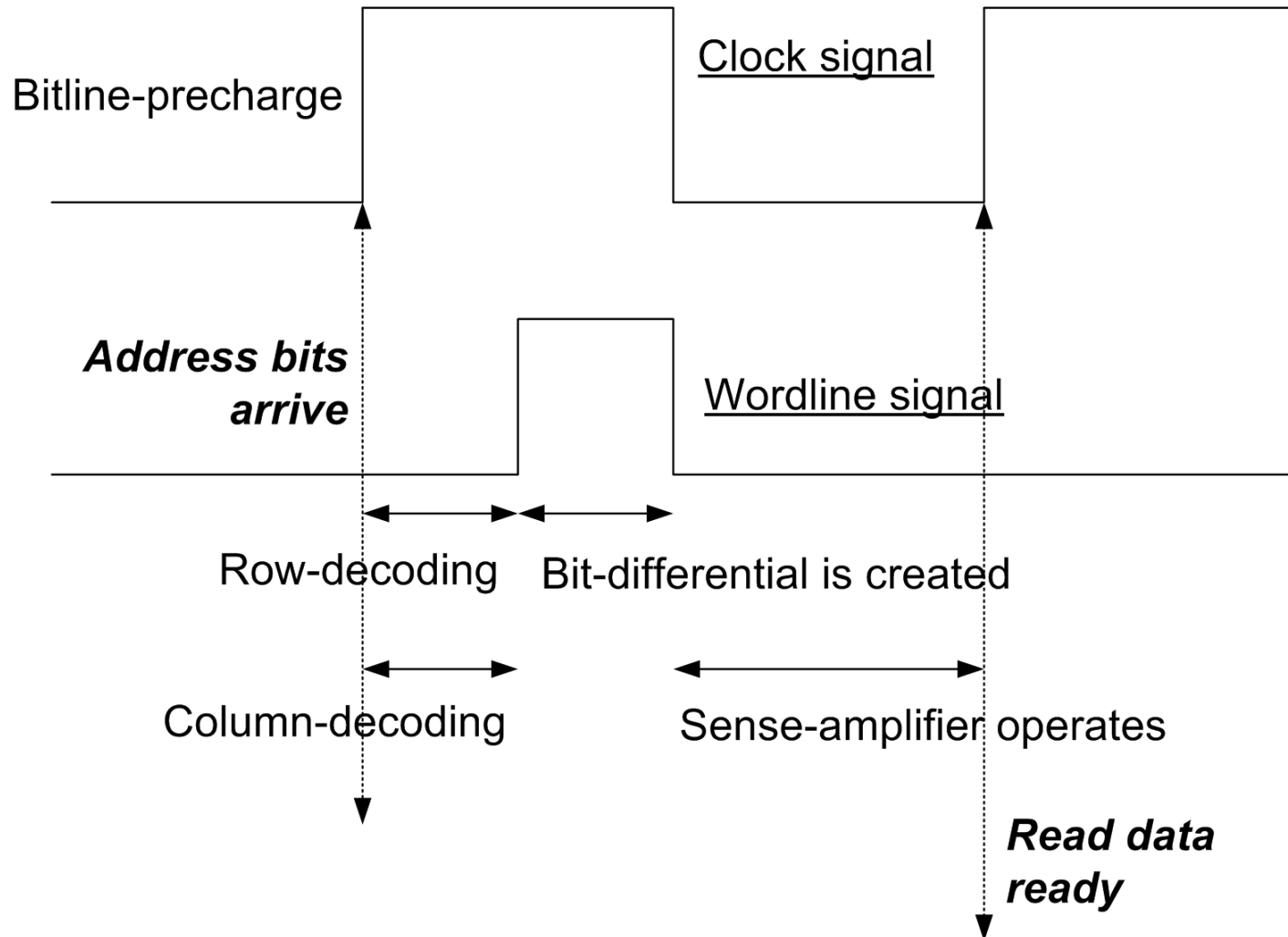

# *Final Report*

- Results Required:
  - Use the modular design and demonstrate reliable read functionality
  - Demonstrate reliable write functionality
  - Power Consumption vs. VDD & Temperature

# *Final Report*

- You are free to adopt any multiplier architecture
- Report the chosen architecture
- Worst-case delay should be less than 1 ns
- Results Required:
  - Show the modular implementation of multiplier
  - Demonstrate proper functionality
  - Plot Delay vs. Supply voltage
  - Plot Delay vs. Temperature



# *Final Report*

- You are free to choose any design style for D FFs
- Setup time  $< 15\%$  of CLK period
- CLK-Q delay  $< 10\%$  of CLK period
- Do not unnecessarily upsize the devices in the latch, it will increase power dissipation
  - Plot CLK-Q delay vs. Supply Voltage
  - Plot CLK-Q delay vs. Temperature
  - Plot Power consumption vs. Clock Frequency

# *Final Report*

- Using the D FFs, implement parallel-in-parallel-out (PIPO) registers
- Implement 4-bit and 9-bit PIPO registers
- Report the modular design and demonstrate proper functionality for a CLK period  $< 1\text{ns}$ 
  - Plot Power Consumption vs. Supply Voltage
  - Plot Power Consumption vs. CLK period
  - Plot Max. operating frequency vs. Supply Voltage

# *Final Report Template*

- Final report is the most critical part of this project
- Find the template of final report on BB
- Final report should combine the summary of the entire project
- Final report should be professionally written and should include properly drawn figure (no screenshots from Cadence, draw schematic figures manually)