

ECE 467 Project #2

Olivier Innocent

Robert Ciesielski

Ryn Stewart

Joseph Riem

Table of Contents

Static CMOS Full Adder	4
Implementation	4
Functionality Verification	5
Required Tests	6
Delay vs. Supply Voltage (with 10f F capacitors)	6
Delay vs. Temperature	7
Leakage Current vs. Supply Voltage Change	8
Leakage Current vs. Temperature Change	9
Transmission Gate Full Adder	10
Implementation	10
Functionality Verification	11
Required Tests	12
Delay vs. Supply Voltage	12
Delay vs. Temperature	13
Leakage Current vs. Supply Voltage Change	14
Leakage Current vs. Temperature Change	15
Choosing 1 Bit adder	16
Area vs. Delay Analysis of 1 bit adders	16
8 Bit Ripple Carry Adder	16
Implementation	16
Functionality Verification(Marked as seen on graph)	17
Required Tests	18
Delay vs. Supply Voltage	18
Delay vs. Temperature	19
Leakage Current vs. Supply Voltage Change	20
Leakage Current vs. Temperature Change	21
8 Bit Carry Select Adder	22
Implementation	22
Functionality Verification	23
Required Tests	25
Delay vs. Supply Voltage	25
Delay vs. Temperature	26
Leakage Current vs. Supply Voltage Change	27
Leakage Current vs. Temperature Change	28
Optimizing One of the 8 Bit Adders	29
Area vs. Delay Analysis of 8 bit adders	29
8-bit adder set-up	29

Appendix A



31

Work Distribution

31


Static CMOS Full Adder

1. Implementation

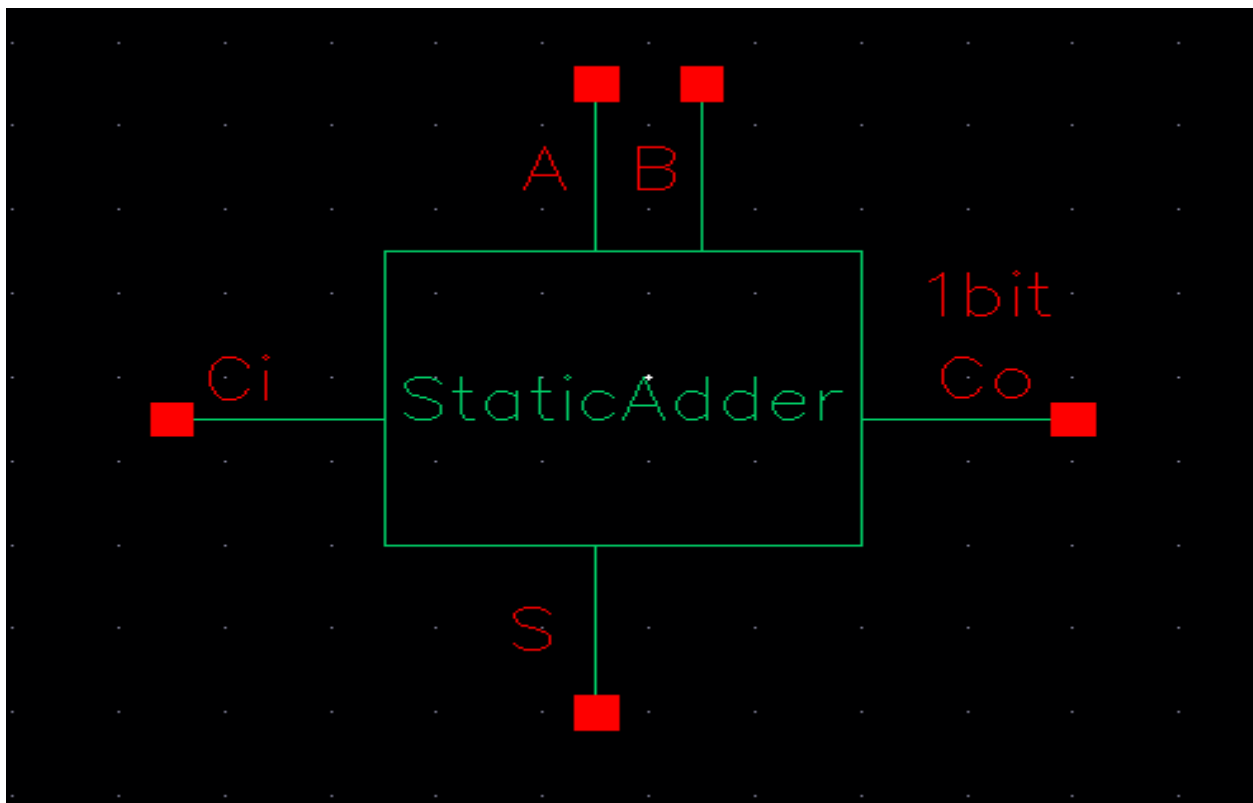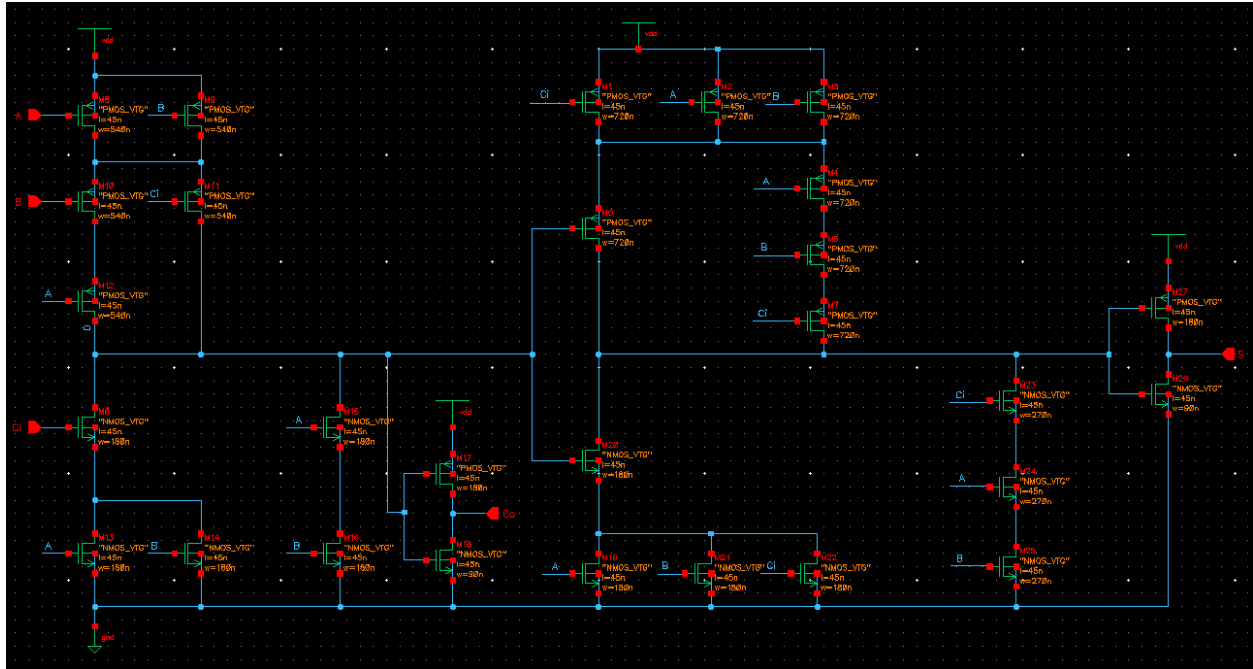


2. Functionality Verification

Test setup:

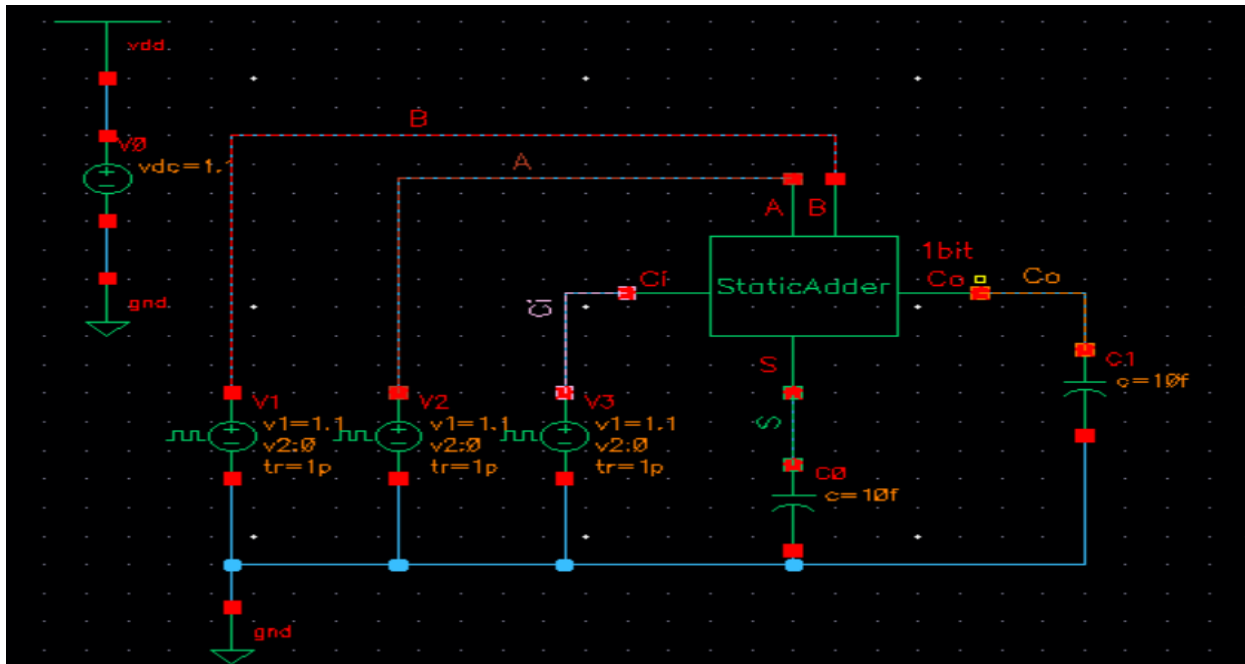

Simulation Results:

 


3. Required Tests

Worst case delay is found at S when A, B switch from high to low and Ci switches low to high.


a. Delay vs. Supply Voltage (with 10f F capacitors)

Voltage(V)	0.9	1.0	1.1	1.2
$t_p(\text{ns})$	0.324	0.23953	0.192	0.14304

 


b. Delay vs. Temperature

Temperature(°C)	t_p (ns)
0°C	0.16043
25°C	0.192
50°C	0.22963
75°C	0.26945
100°C	0.31746

 

c. Leakage Current vs. Supply Voltage Change


Voltage (V)	0.9	1.0	1.1	1.2
Leakage Current (nA)	1.12926	2.36784	8.38502	54.6038

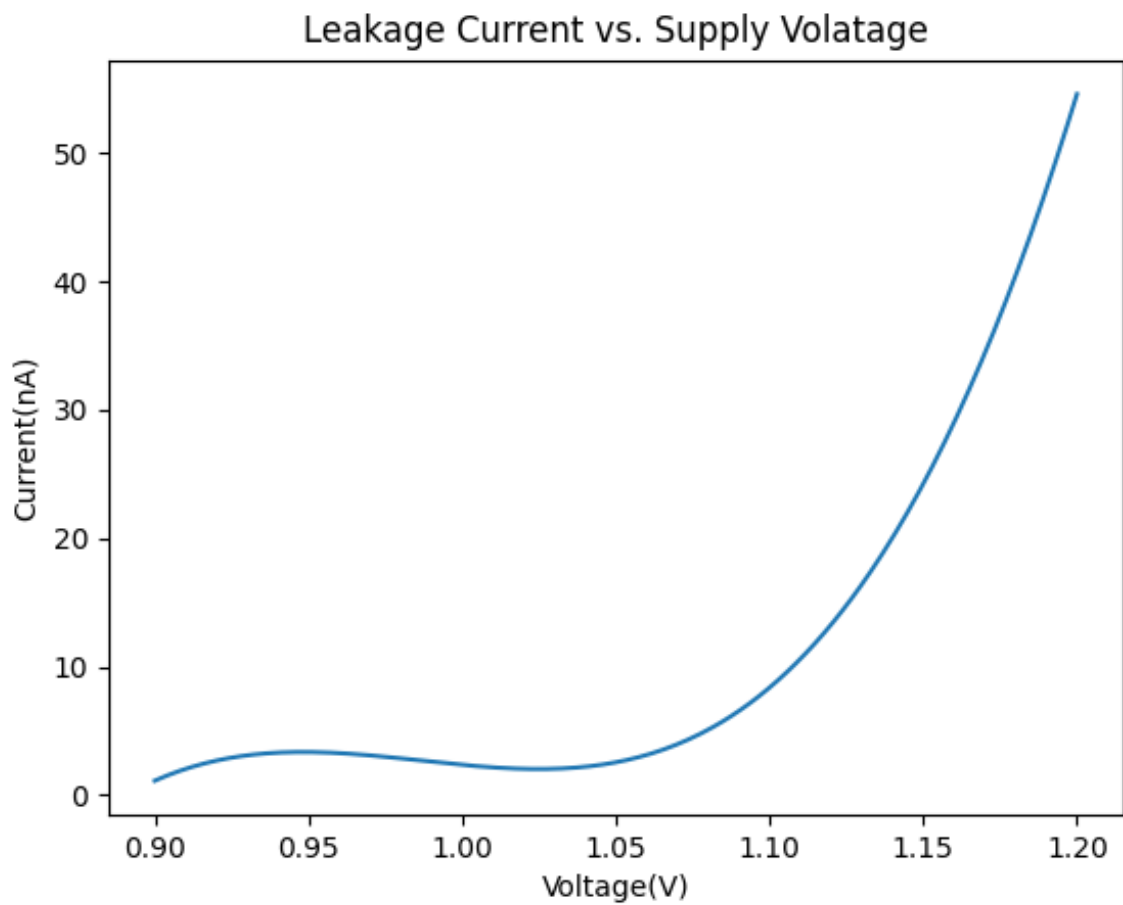

d. Leakage Current vs. Temperature Change



Supply voltage set to 1.1V


Temperature(°C)	Leakage current (nA)
0°C	4.46859
25°C	8.38502
50°C	14.2795
75°C	22.533
100°C	33.458

 

Transmission Gate Full Adder

1. Implementation

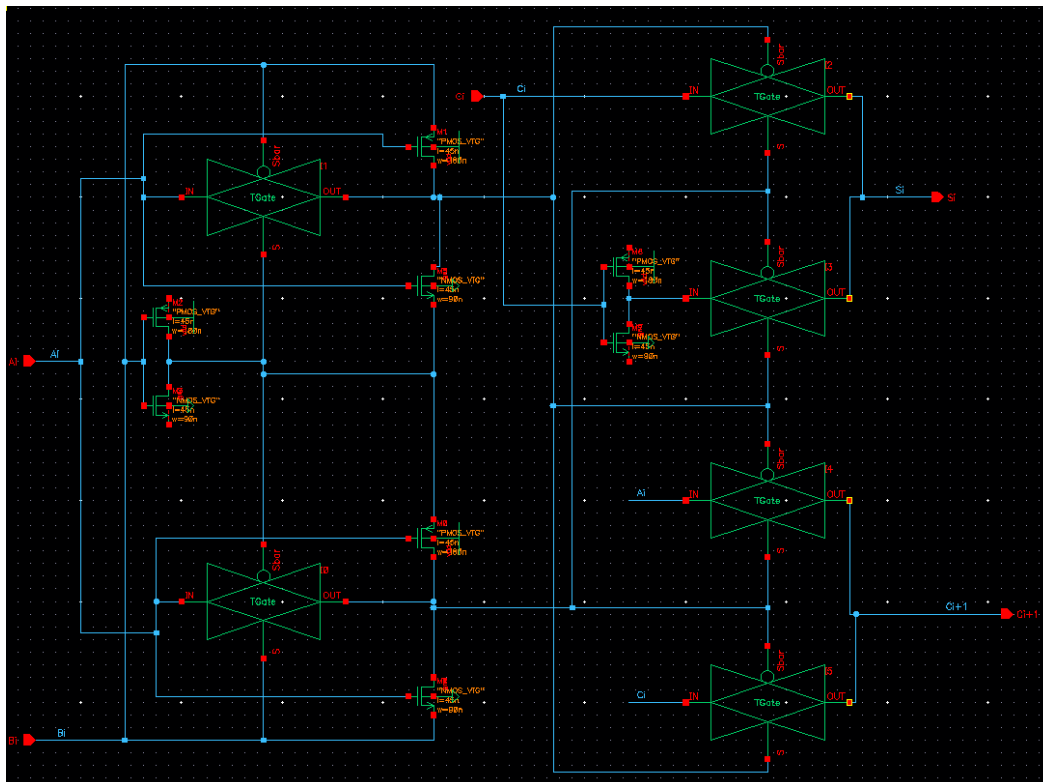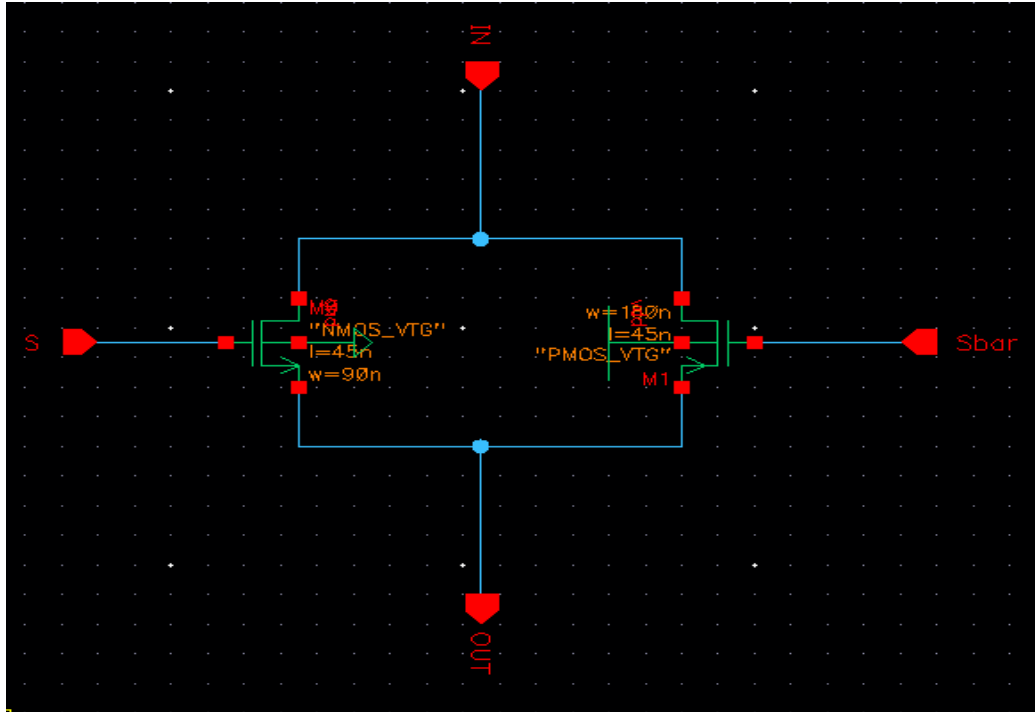


 

3. Required Tests


a. Delay vs. Supply Voltage

Voltage(V)	0.9	1.0	1.1	1.2
$t_p(\text{ns})$	0.45705	0.26228	0.19077	0.13973

 


b. Delay vs. Temperature

Temperature(°C)	$t_p(\text{ns})$
0°C	0.20623
25°C	0.25194
50°C	0.30262
75°C	0.35853
100°C	0.43288

 


c. Leakage Current vs. Supply Voltage Change

Voltage(V)	0.9	1.0	1.1	1.2
Leakage Current	1.0689	2.0243	3.8423	7.3290

 

d. Leakage Current vs. Temperature Change

Temperature(°C)	Leakage current(nA)
0°C	2.2857
25°C	3.8423
50°C	5.9566
75°C	8.6686
100°C	11.9995

 



Choosing 1 Bit adder

1. Area vs. Delay Analysis of 1 bit adders

TYPE	AREA	DELAY (ns)
Static CMOS FA	481.95 μm^2	0.192 (supply voltage of 1.1V)
Transmission Gate FA	121.5 μm^2	0.252(supply voltage of 1.1V)


8 Bit Ripple Carry Adder

1. Implementation

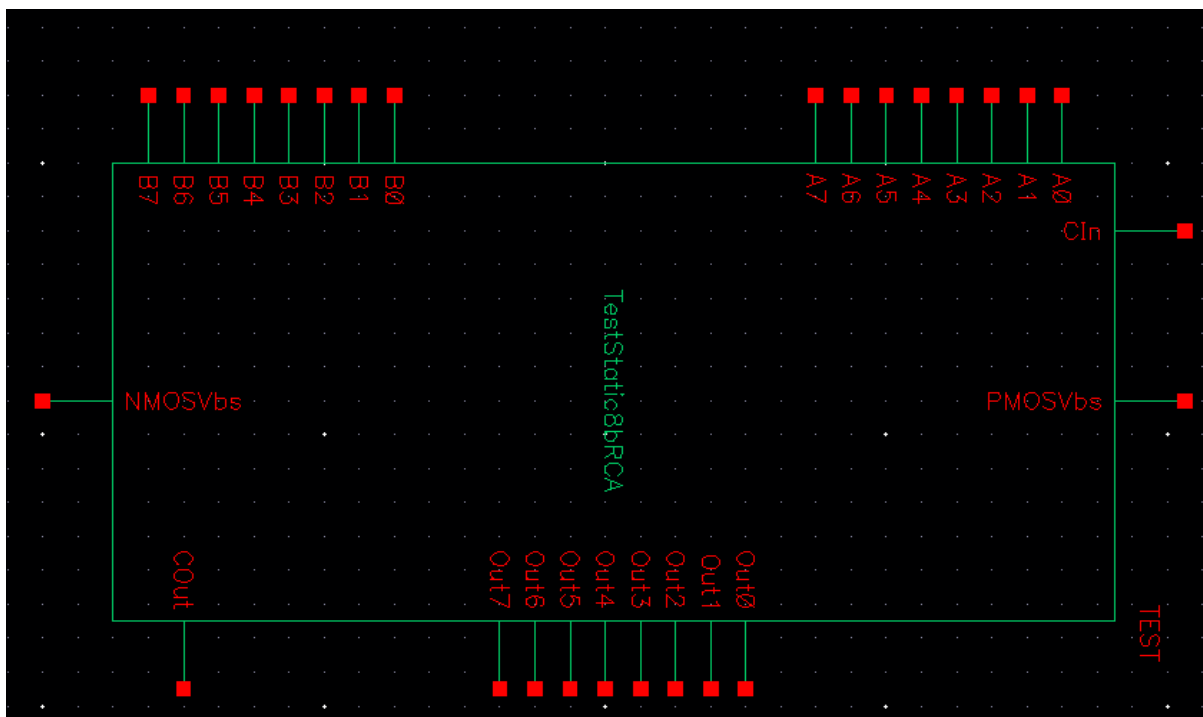 


2. Functionality Verification(Marked as seen on graph)

 
a. $82(01010010)+97(01100001)+0 = 010110011(179)$



 b. $48(00110000)+33(00100001)+0 = 001010001(81)$



 c. $214(11010110)+129(10000001)+1 = 101011000(344)$




Worst case delay shown at the end of the report in the optimizing section.

3. Required Tests


a. Delay vs. Supply Voltage

Voltage(V)	0.9	1.0	1.1	1.2
$t_p(\text{ns})$	1.23922	.885655	.629955	.578895

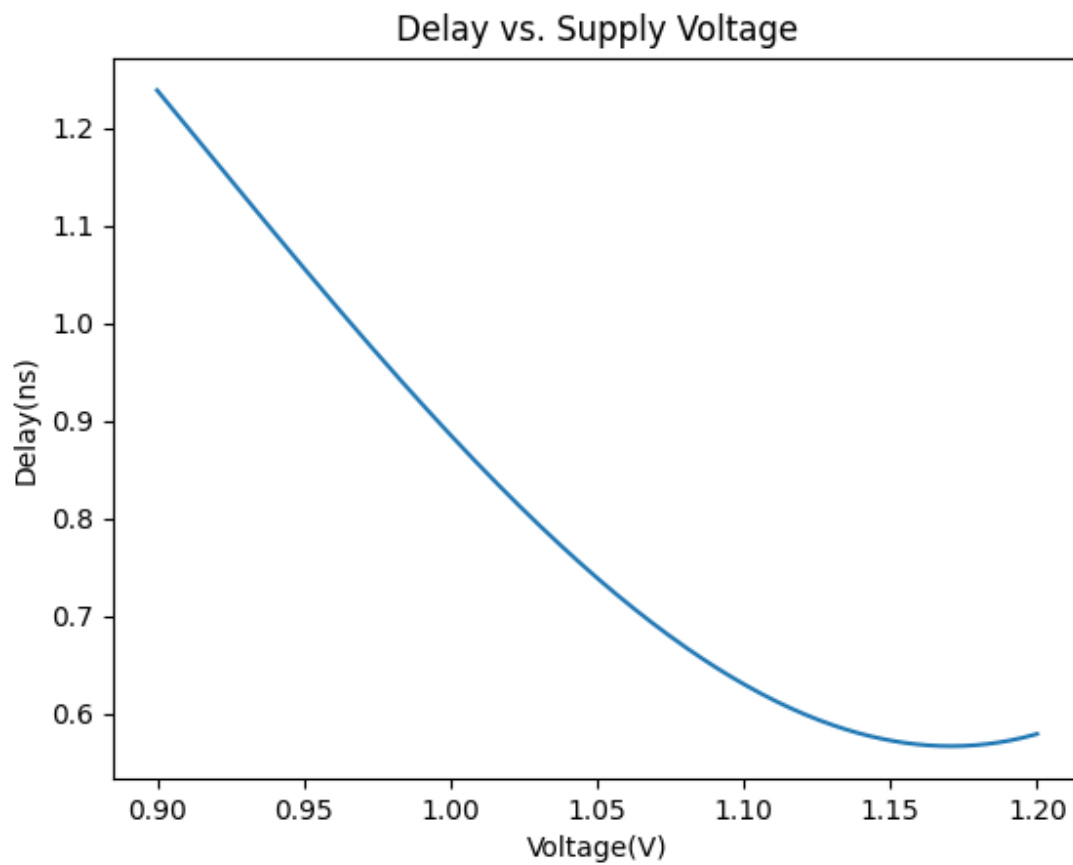


b. Delay vs. Temperature

Temperature(°C)	$t_p(\text{ns})$
0°C	0.600575
25°C	0.629955
50°C	0.803205
75°C	0.92252
100°C	1.052595

 


c. Leakage Current vs. Supply Voltage Change

Voltage(V)	0.9	1.0	1.1	1.2
Leakage Current(nA)	15.4	25.285	41.649	68.783

 

d. Leakage Current vs. Temperature Change



Temperature(°C)	Leakage current(nA)
0°C	29.296
25°C	41.649
50°C	73.651
75°C	120.155
100°C	183.746

 

8 Bit Carry Select Adder

 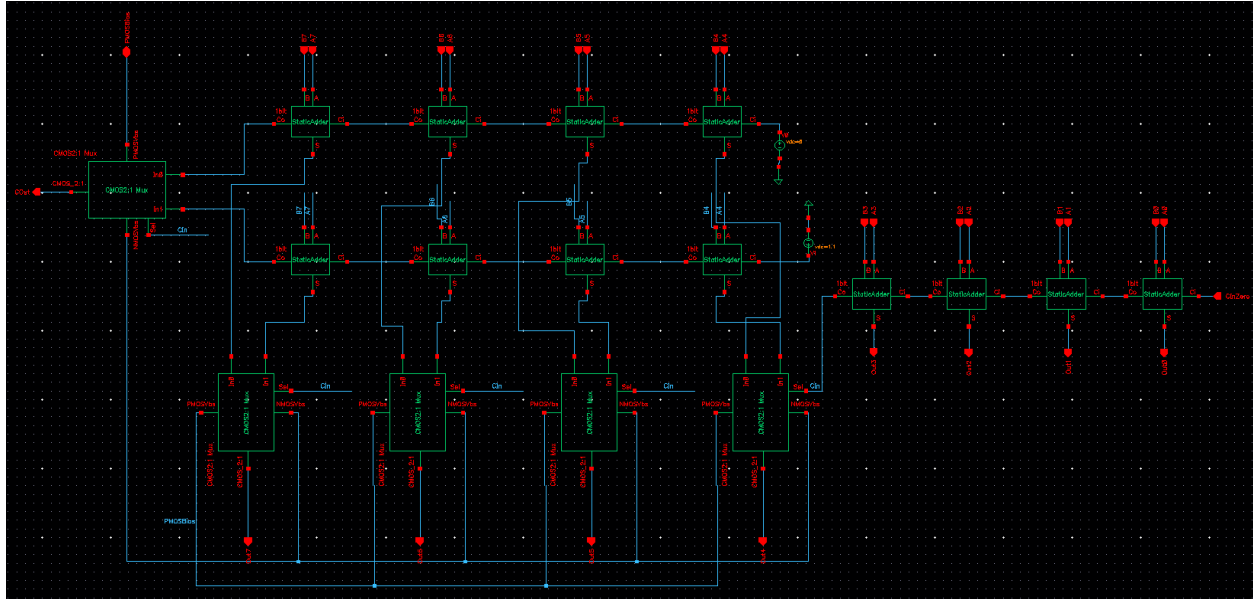
1. Implementation

Done with Static CMOS implementation of a 1 bit full adder. There are a total of 12 full adders and 5 2:1 mux.




2. Functionality Verification


Testing setup:

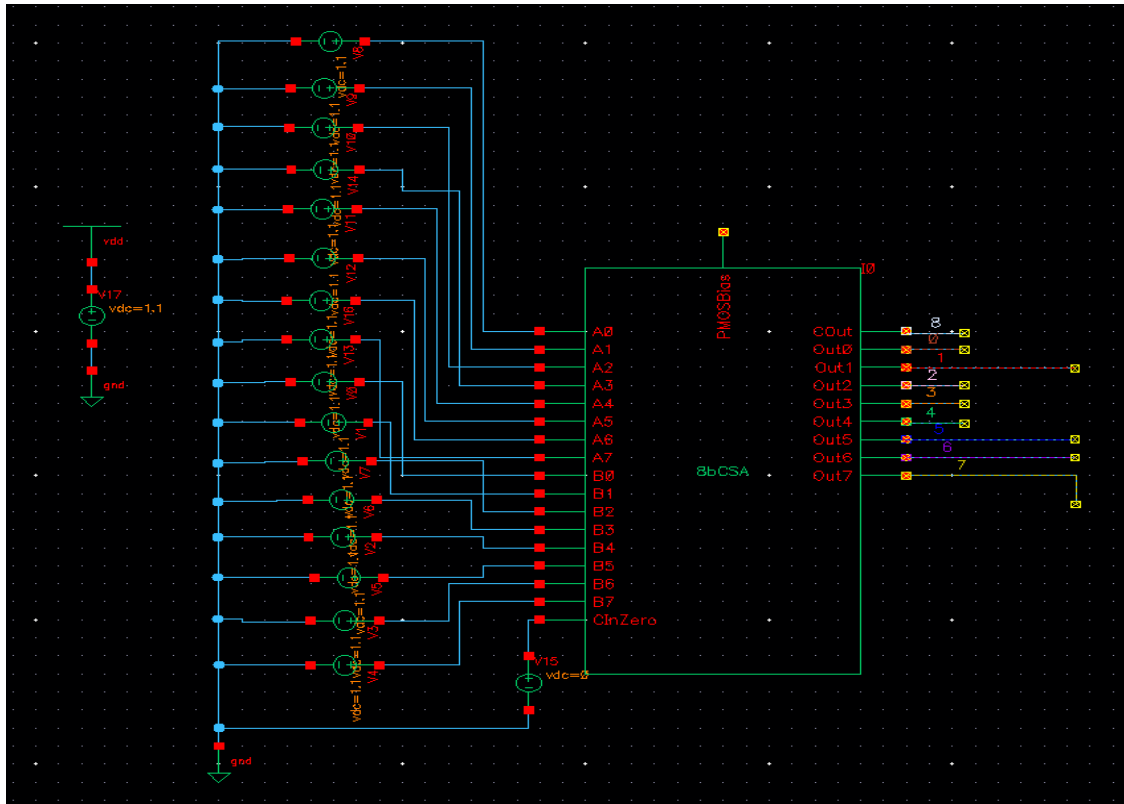

 
a. $(255)11111111 + (255)11111111 + 0 = 111111110(510)$



 b. $48(00110000)+33(00100001)+0 = 001010001(81)$



 c. $214(11010110)+129(10000001)+1 = 101011000(344)$




Worst case delay shown at the end of the report in the optimizing section.

3. Required Tests


a. Delay vs. Supply Voltage

Voltage(V)	0.9	1.0	1.1	1.2
$t_p(\text{ns})$	0.47643	0.33678	0.2618	0.21753

 


b. Delay vs. Temperature

Temperature(°C)	t_p (ns)
0°C	0.2256
25°C	0.2618
50°C	0.3034
75°C	0.3502
100°C	0.4017

 


c. Leakage Current vs. Supply Voltage Change

Voltage(V)	0.9	1.0	1.1	1.2
Leakage Current(nA)	72.6	128.181	260.186	933.721

 

d. Leakage Current vs. Temperature Change

Temperature(°C)	Leakage current(nA)
0°C	144.5082
25°C	260.186
50°C	428.210
75°C	636.542
100°C	867.856

 

Optimizing One of the 8 Bit Adders


1. Area vs. Delay Analysis of 8 bit adders

- Delay is measured at the worst case which was when one input was 255 and the other flipped to one.

TYPE	AREA	DELAY(ps)
8 bit Ripple Carry Adder	3.8556 mm ²	479.805 (optimized at 1.2 V)
8 bit Carry Select Adder	5.9657 mm ²	260.186 (at 1.1V)

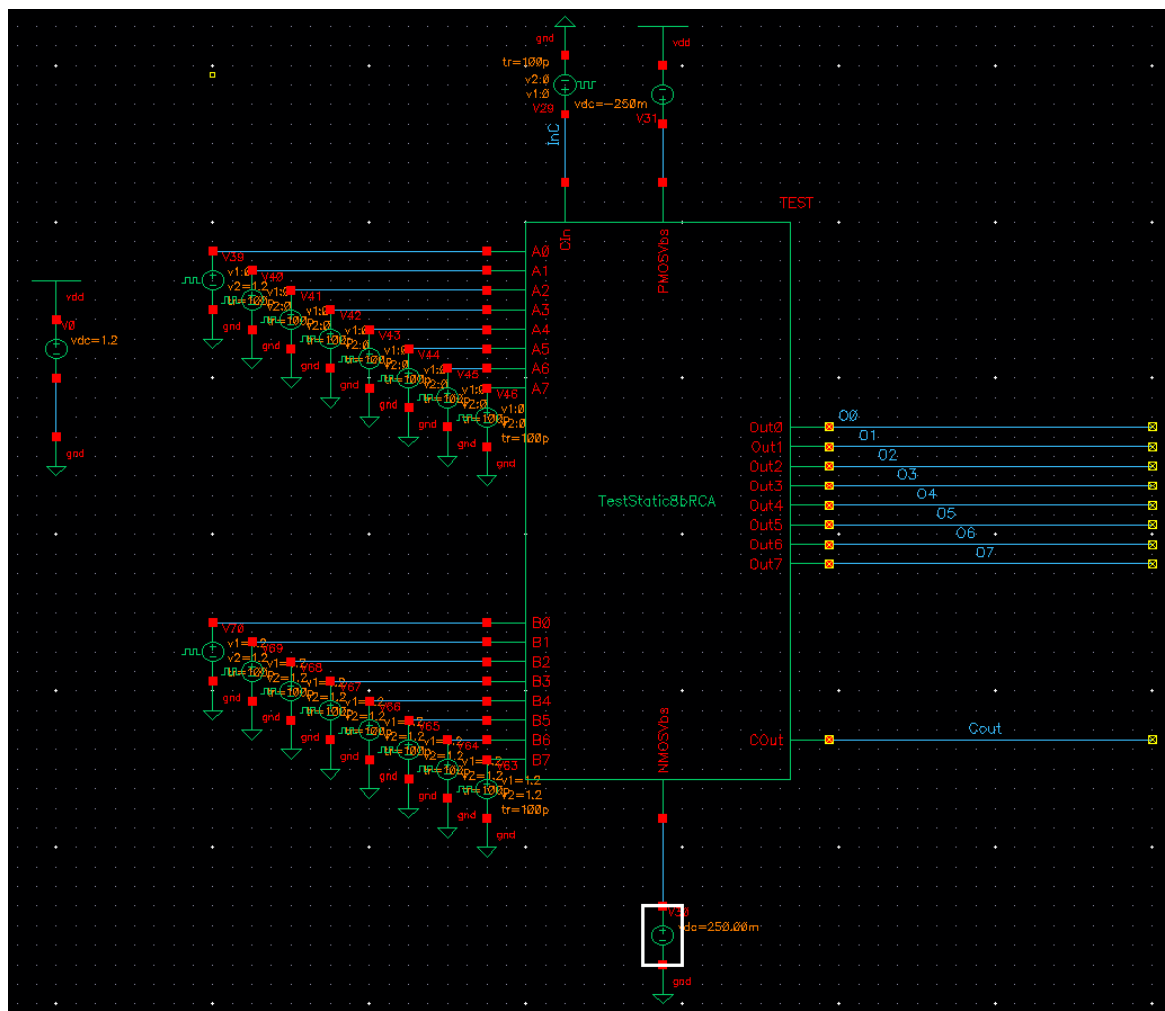2. 8-bit adder set-up

Parameters: Vdd = 1.2V, PMOSVb = 0.95V, NMOSVb = 0.25V, A = 00000001, B = 11111111, CIn = 0, T = 25C




3. Simulation results


Transient Response

Tue Nov 17 12:56:41 2020 1

Name	Vis
/Cout	<input checked="" type="checkbox"/>
/In	<input checked="" type="checkbox"/>

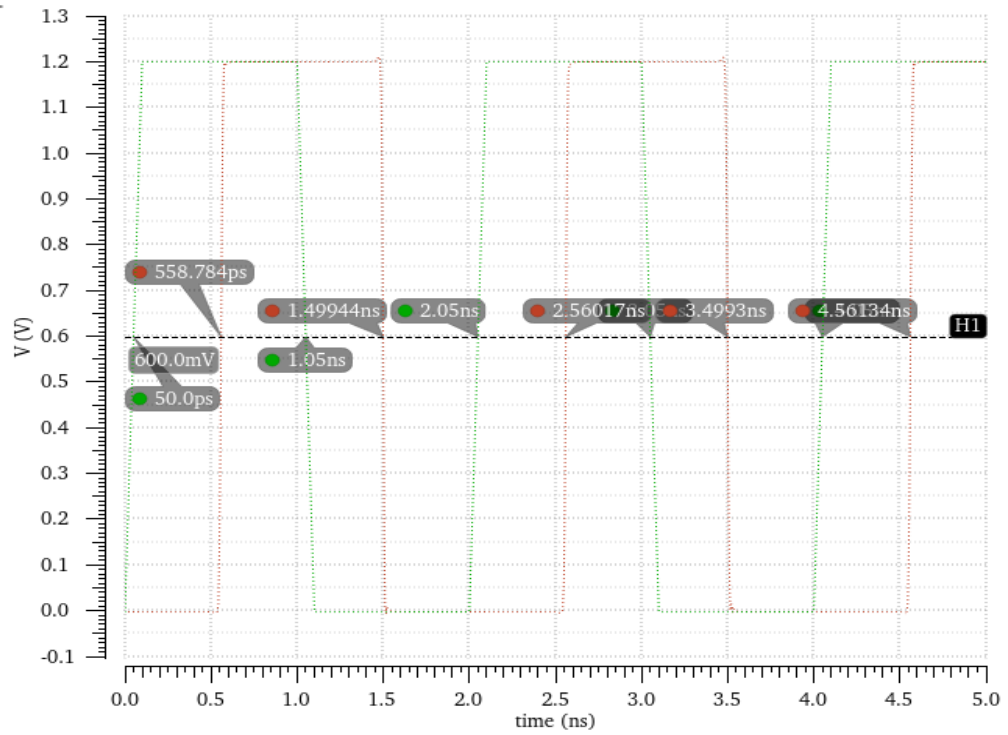

Name	Vis
/O0	<input checked="" type="checkbox"/>
/O1	<input checked="" type="checkbox"/>
/O2	<input checked="" type="checkbox"/>
/O3	<input checked="" type="checkbox"/>
/O4	<input checked="" type="checkbox"/>
/O5	<input checked="" type="checkbox"/>
/O6	<input checked="" type="checkbox"/>
/O7	<input checked="" type="checkbox"/>
/In	<input checked="" type="checkbox"/>

 

Appendix A

Work Distribution

Olivier Innocent	Report formatting and graphs
Joseph Riem	Ripple Carry Adder: <ul style="list-style-type: none"> • All parts Carry Select Adder: <ul style="list-style-type: none"> • Initial design work Optimization of 8 bit adder

Ryn Stewart	Static CMOS Full Adder: <ul style="list-style-type: none">• All Parts Carry Select Adder: <ul style="list-style-type: none">• Implementation• Functionality verification
Robert Ciesielski	Transition Gate Full Adder: <ul style="list-style-type: none">• All parts Carry Select Adder: <ul style="list-style-type: none">• All tests